
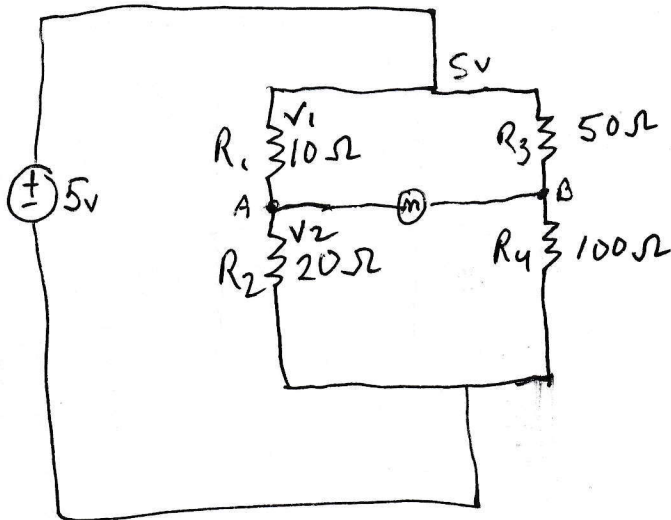
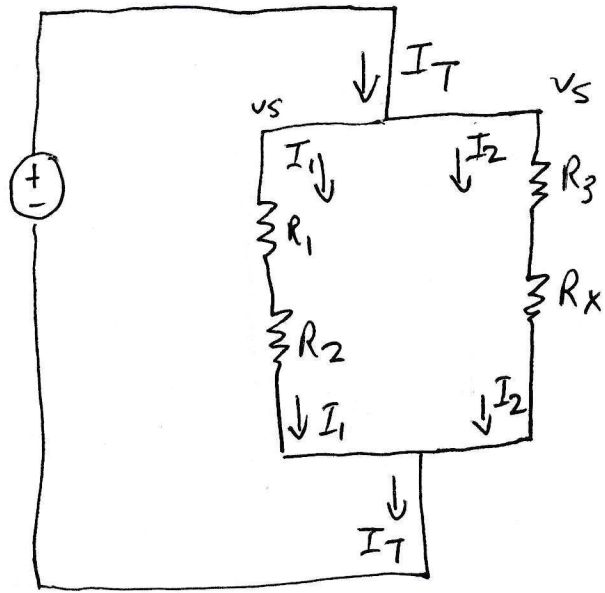


# Wheatstone Bridge

①

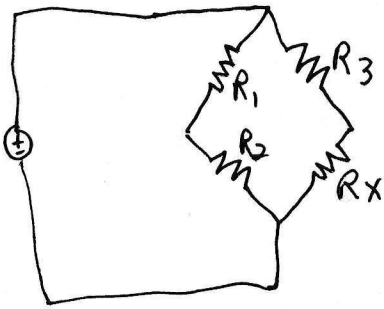

Ohms Law  
 $V = IR$

1:2 ratio

$$R_1 = \frac{10\Omega}{20\Omega} = \frac{1}{2}$$

$$R_3 = \frac{50}{100} = \frac{1}{2}$$

$$V_1 = \frac{R_1}{R_1 + R_2} \cdot V_S = \frac{10\Omega}{10\Omega + 20\Omega} = \frac{10\Omega}{30\Omega} = \frac{1}{3} \cdot V_S = \frac{1}{3} \cdot 5V = 1.67V$$

1.67  
 $\frac{5 \times 2}{3}$

$$V_2 = \frac{R_2}{R_1 + R_2} \cdot V_S = \frac{20\Omega}{10\Omega + 20\Omega} = \frac{20\Omega}{30\Omega} \cdot V_S = \frac{2}{3} (5V) = 3.33V$$

$$V_3 = \frac{R_3}{R_3 + R_4} \cdot V_S = \frac{50}{50 + 100} = \frac{50}{150} \cdot V_S = \frac{1}{3} \cdot V_S = 1.67V$$

$$V_4 = \frac{R_4}{R_3 + R_4} \cdot V_S = \frac{100}{50 + 100} = \frac{100}{150} = \frac{2}{3} \cdot V_S = 3.33V$$


$$V_A = 3.33V$$

$$V_B = 3.33V$$

$$V_A - V_B = 0V$$

# Wheatstone Bridge

(2)

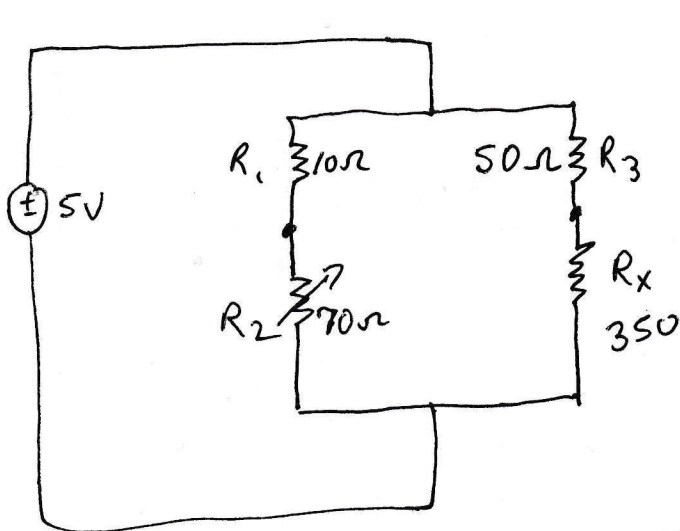

$$\frac{R_1}{R_2} = \frac{R_3}{R_x}$$


$$\frac{10}{70} = \frac{50}{350} = \frac{1}{7} = \frac{5}{35} = \frac{1}{7}$$

When a Bridge is Balanced, Ratio is the same.

$$\boxed{\frac{R_1}{R_2} = \frac{R_3}{R_x}}$$

$$R_x = \frac{R_2}{R_1} \cdot R_3 = \frac{70}{10} \cdot 50 = \frac{3500}{10} = 350\Omega$$

# In the Lab

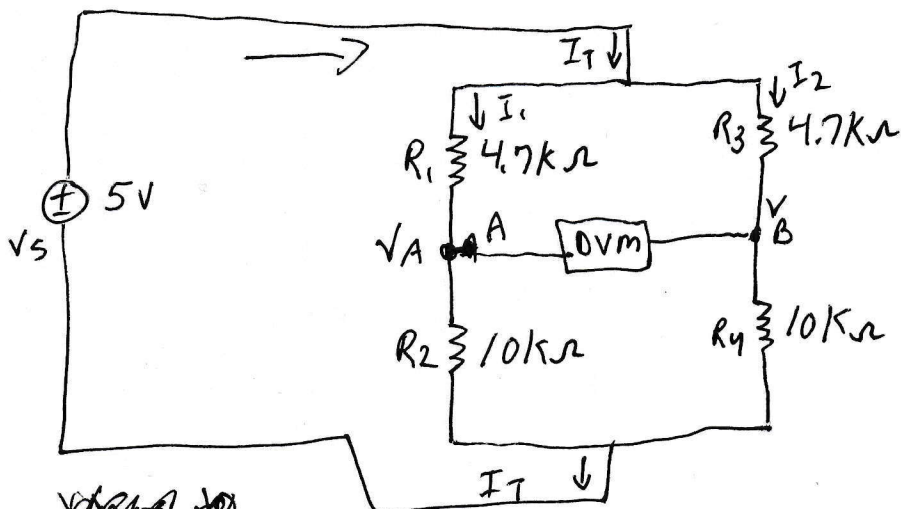

Build circuits with rich.com

$$V_A = 5V \cdot \frac{10,000\Omega}{14,700\Omega} = 3.40V, \quad V_A = V_S \cdot \left( \frac{R_2}{R_1 + R_2} \right)$$


$$V_B = 5 \cdot \frac{10,000\Omega}{14,700\Omega} = 3.40V, \quad V_B = V_S \cdot \left( \frac{R_4}{R_3 + R_4} \right)$$

$$V_{R1} = V_S \cdot \frac{R_1}{R_1 + R_2} = 1.6V$$

$$V_{R2} = V_S \cdot \frac{R_2}{R_1 + R_2} = 3.40V$$

$$V_{R3} = V_S \cdot \frac{R_3}{R_3 + R_4} = 1.6V$$
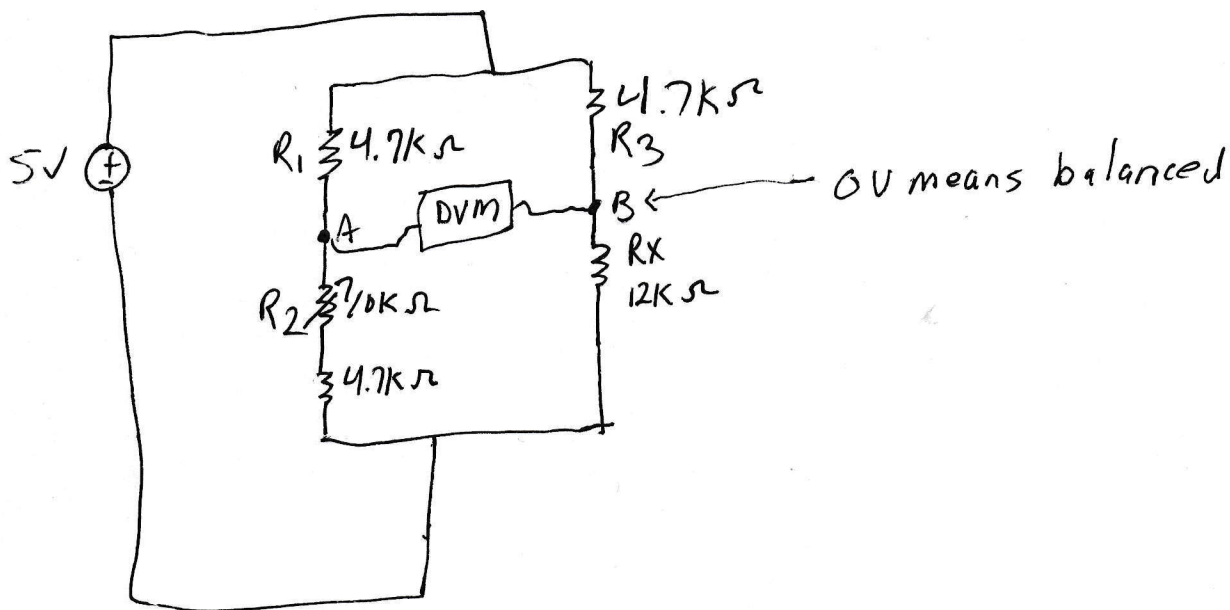
$$V_{R4} = V_S \cdot \frac{R_4}{R_3 + R_4} = 3.40V$$



(4)

Encouraging Bible Verse:

John 3:16

"For God so loved the world, that he gave his only begotten Son, that whosoever believeth in him should not perish, but have everlasting life."