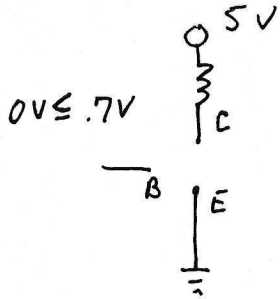


# OPTO-Coupler


Transistor  
2N2222

Cutoff




OFF switch  
OPEN circuit

Active



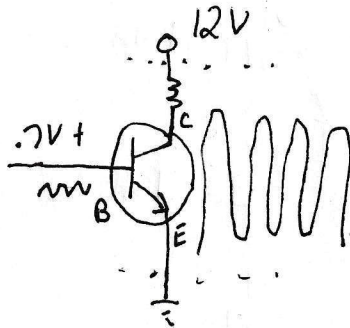


Amplifier  
 $B = \text{Gain}$   
 $\frac{I_c}{I_B}$

Saturation

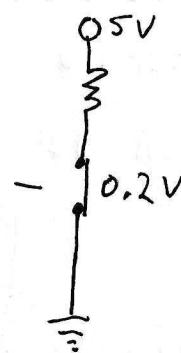

ON switch  
closed circuit

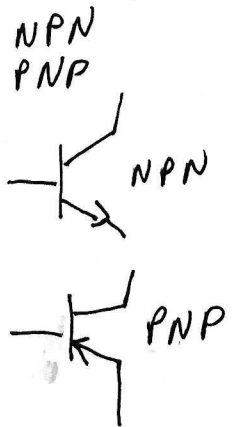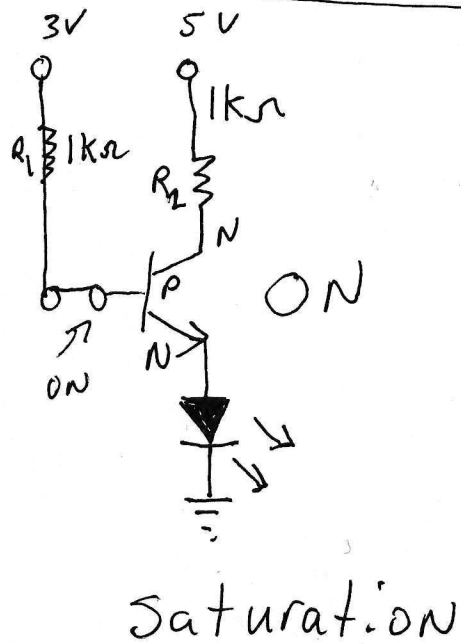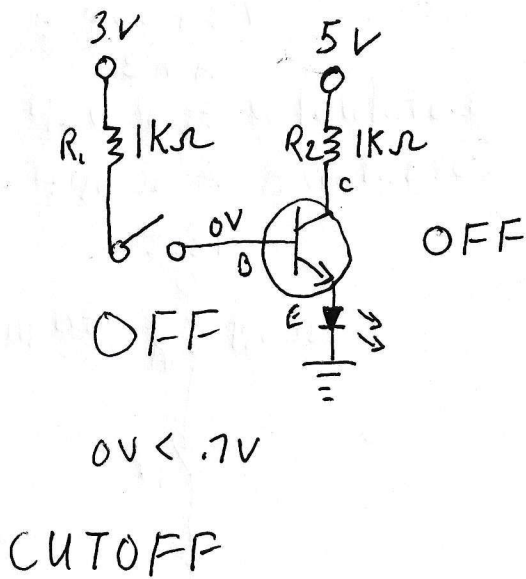


# OPTO - Coupler 4N35

②

3.3V

5V

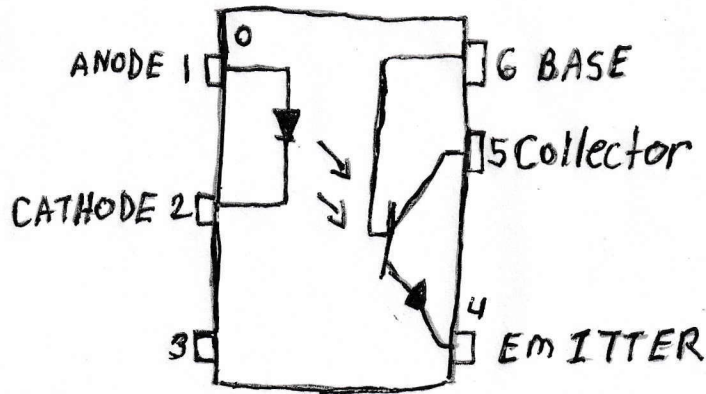

Forward Voltage is 1.2V.

$$R_1 = \frac{V_{in} - 1.2V}{5mA}$$

$$R_1 = \frac{3.3V - 1.2V}{5mA} =$$



$R_1 = 420\Omega \rightarrow$  Calculated

$R_1 = 470\Omega \rightarrow$  Available

I Limit is 10-20mA.

Choose 5mA for reliability

$$V = IR$$

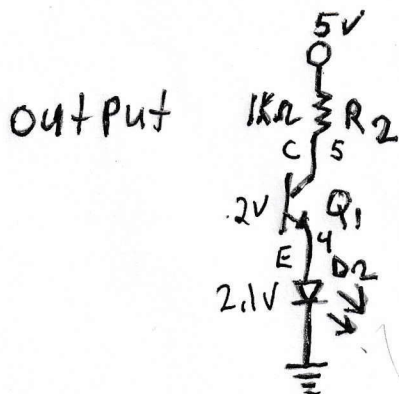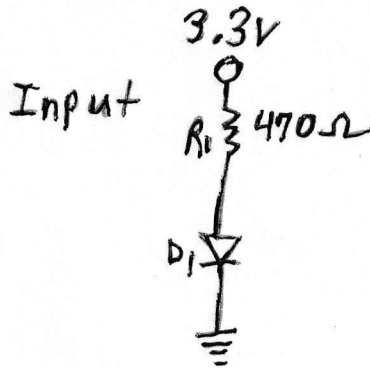

$V_{cc} = 5V$   
LED = 2.1V  
 $Q_1 = 0.2V$

Current limit  
1-5mA

$$R_2 = \frac{5 - 2.1 - 0.2}{3mA} = 900\Omega$$

use  $1k\Omega = 1000\Omega = R_2$

Bible Verse

ISAIAH 41:10

Fear thou not; for I am with thee; be not dismayed; for I am thy God; I will strengthen thee; yea, I will help thee; yea, I will uphold thee with the right hand of my righteousness.