
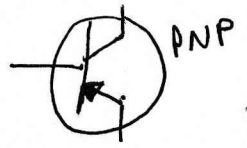


# Transistor Logic

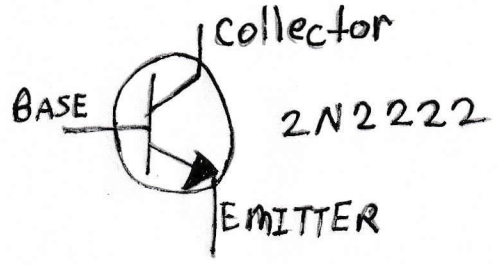


NPN



Truth Table

In	out
0	0
1	1

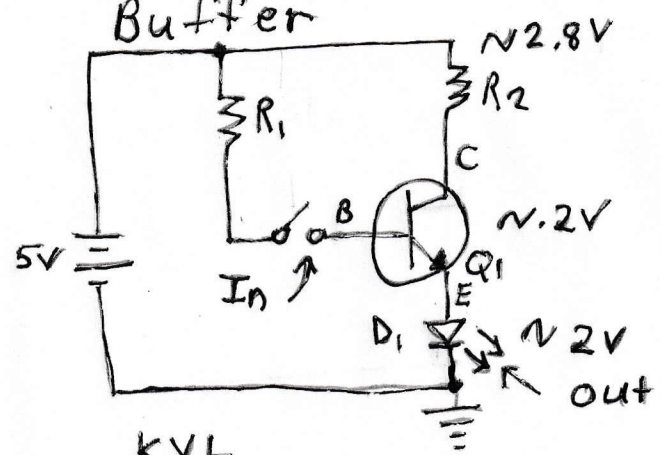

KVL

$$5V = V_{R2} + V_{Q1} + V_{D1}$$

$$V_{R2} = 5V - V_{Q1} - V_{D1}$$

$$V_{R2} = 5V - .2V - 2V = 2.8V$$

$I_{D1}$  should be 10mA since 20mA is the maximum I.

$$V = IR$$


$$R_2 = \frac{V}{I} = \frac{V_{R2}}{I_T} = \frac{2.8V}{10mA} = 280\Omega$$

$R_1$  Calculation

$$V_{BE} = 0.7V$$

KVL

$$V_{BE} = 5V - 0.7V = 4.3V$$

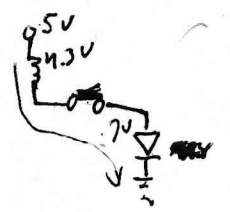

Since we decided we want 10mA  $I_C = 10mA$ .  $\beta$  is 100.


We'll pretend it to be 10.

$$\frac{I_C}{I_B} = 10, I_B = \frac{I_C}{10} = \frac{10mA}{10} = 1mA$$

$$R_1 = \frac{V}{I} = \frac{5 - .7V}{1mA} = 4.3k\Omega$$

Reality  $R_2 = 470\Omega$   
 $R_1 = 4.7k\Omega$

## Inverter

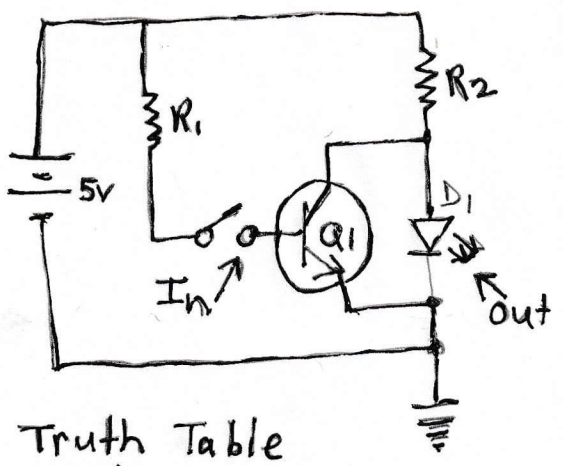


Truth Table

In	Out
0	1
1	0

0 = OFF  
 1 = ON

Cut off Active

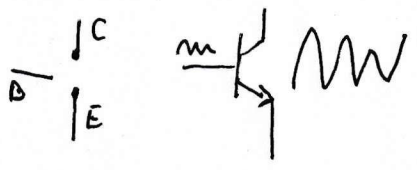


Saturation



# Transistor Logic

## "AND" Gate

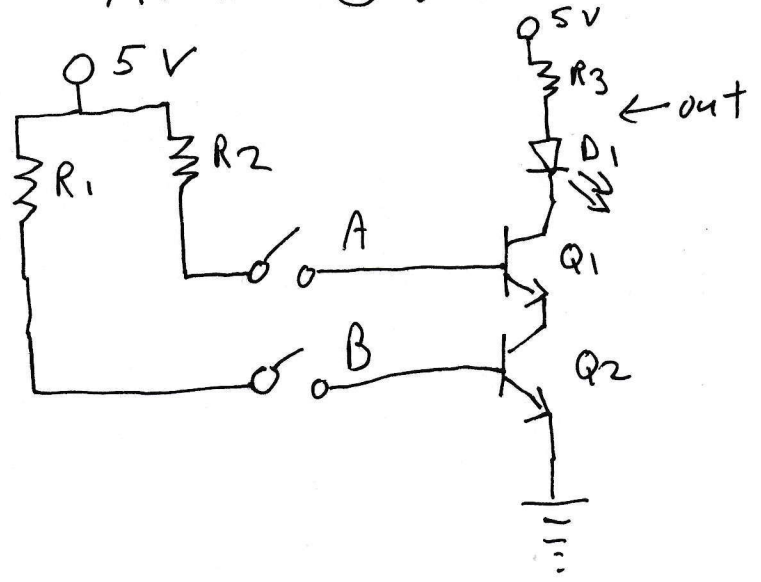


## Truth Table

A	B	out
0	0	0
0	1	0
1	0	0
1	1	1



0 = OFF  
1 = ON


## "NAND" GATE

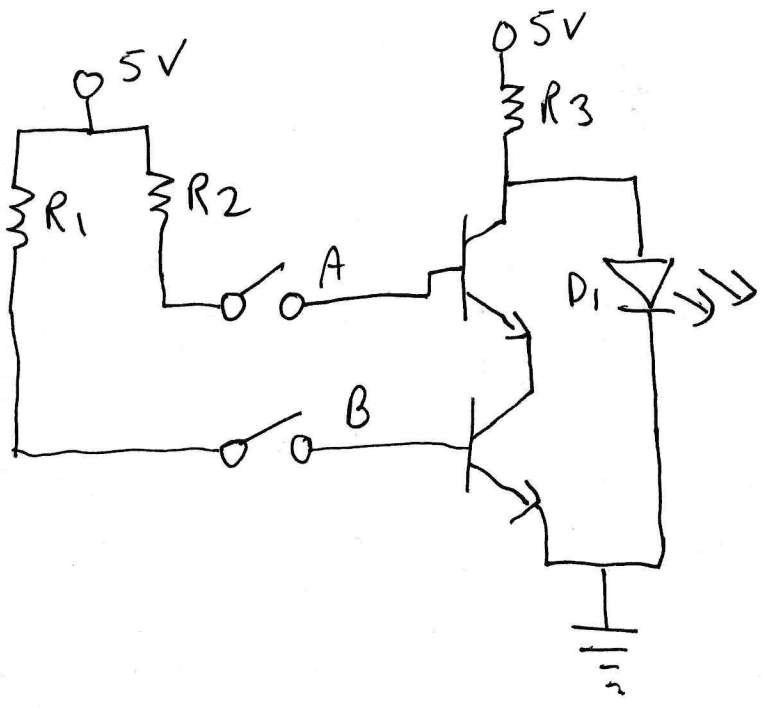

## Truth Table

A	B	out
0	0	1
0	1	1
1	0	1
1	1	0

0 = OFF  
1 = ON

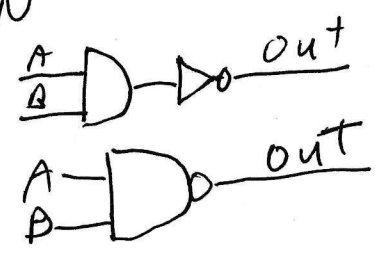

## Psalm 23

### King James Version

23 The Lord is my shepherd; I shall not want.

2 He maketh me to lie down in green pastures: he leadeth me beside the still waters.

3 He restoreth my soul: he leadeth me in the paths of righteousness for his name's sake.

4 Yea, though I walk through the valley of the shadow of death, I will fear no evil: for thou art with me; thy rod and thy staff they comfort me.

5 Thou preparest a table before me in the presence of mine enemies: thou anointest my head with oil; my cup runneth over.

6 Surely goodness and mercy shall follow me all the days of my life: and I will dwell in the house of the Lord for ever.