

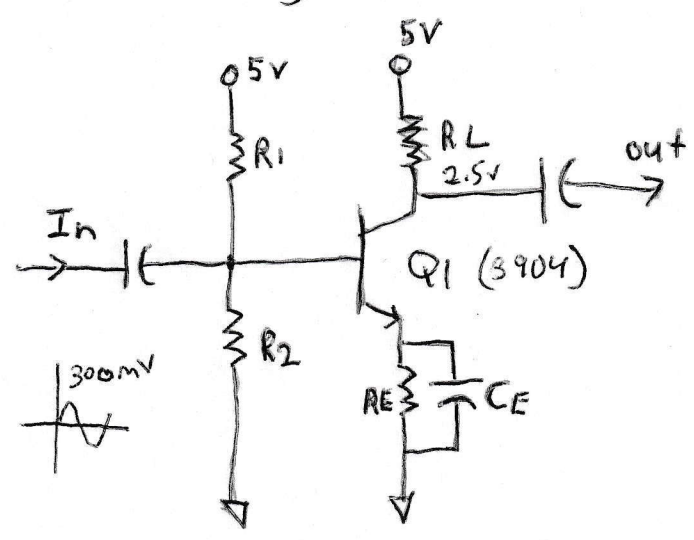






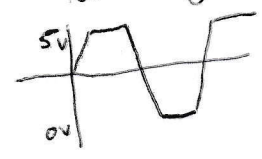
The amazing Semiconductor - Part 5 / Building our first Amplifier



Class A

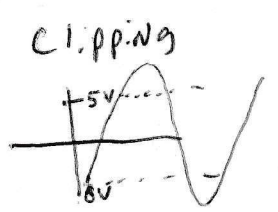

Q point

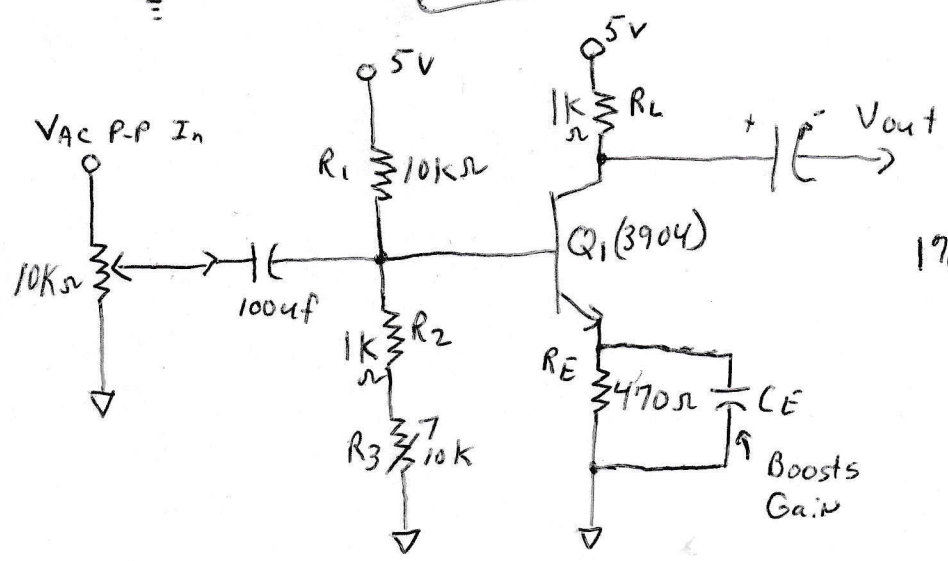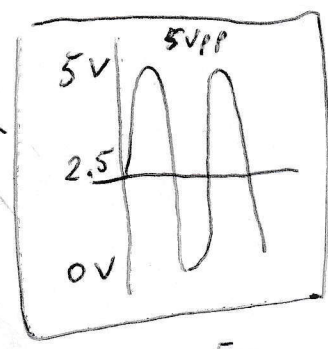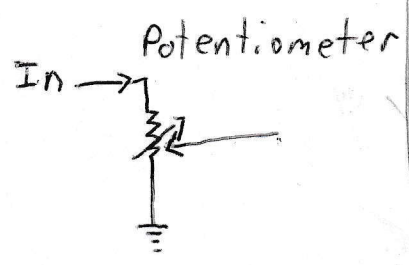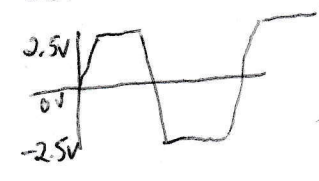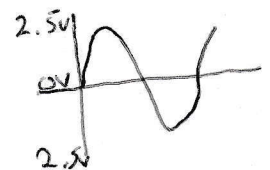

1% tolerance