
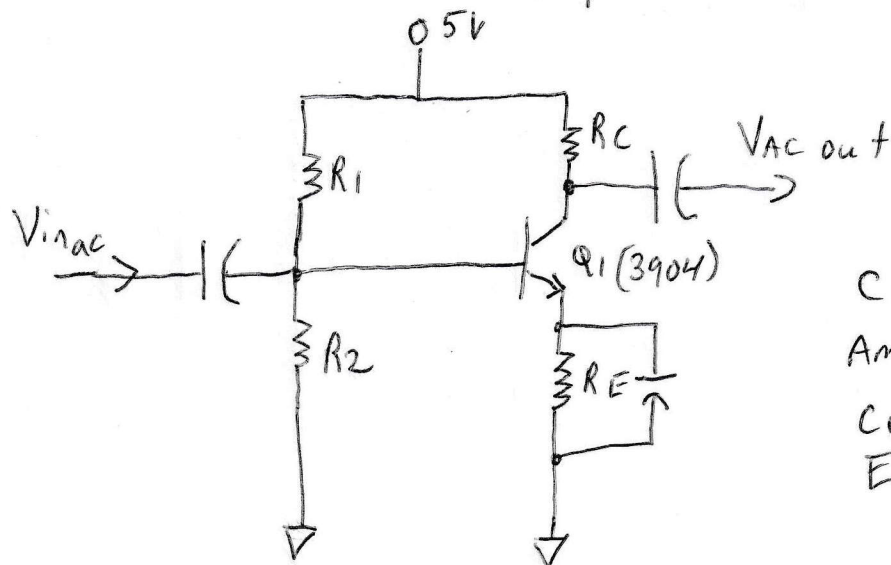


The amazing Semiconductor - Part 6 / Amplifier Design




①

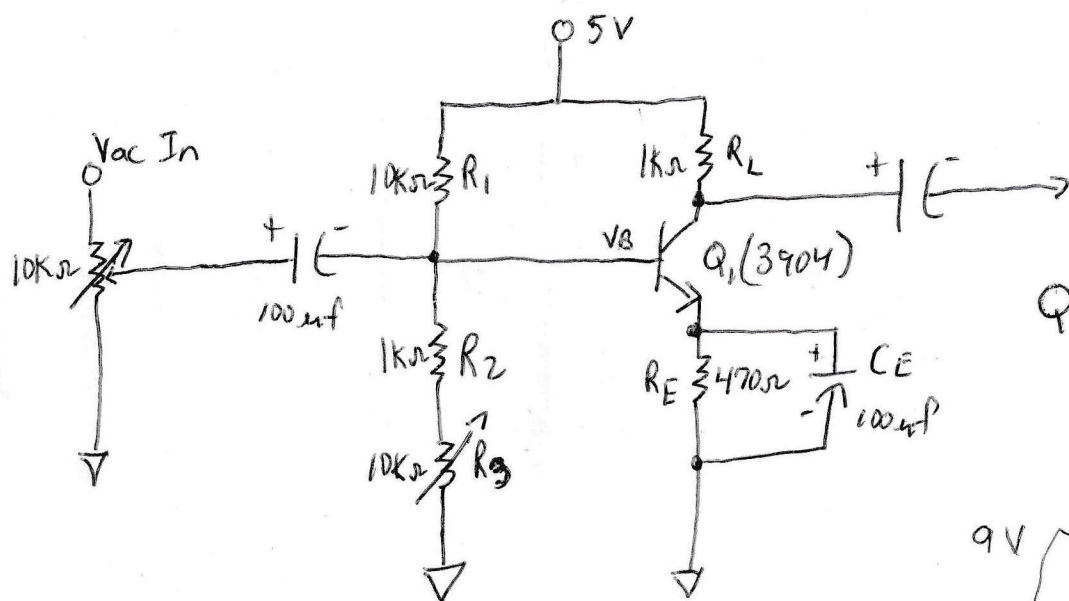

Class A
Amplifier
Common
Em. tter



$Q_{point} = 2.5V$

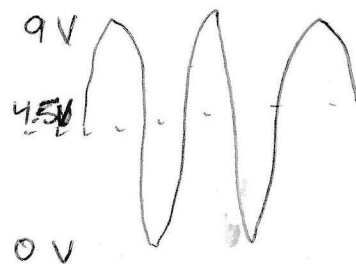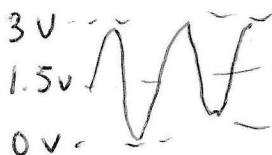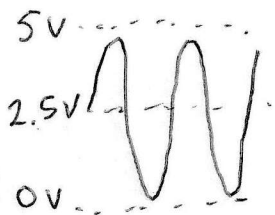

Power = 625mW $V_{max} = 40V_{dc}$ 50-80%
24V as the highest

$Q_{point} = 2.5V$
PWR Supply = 5V

The amazing Semiconductor - Part 6 | Amplifier Design

2

Q point 2.5V

$$I_C \approx I_E = 2.5 \text{ mA}$$

" = 5V

- Low power consumption

- Plenty of gain for a pre-amp

- thermal = cool

- Makes calculations of resistors easier 1k Ω , 470 Ω

$$I_C = 2.5 \text{ mA}$$

$$V = IR, R = \frac{V}{I} = \frac{V_L}{I_C} = \frac{5V - 2.5V}{I_C} = \frac{V_{DC} - V_L}{I_C} = \frac{5 - 2.5}{2.5 \text{ mA}} = \frac{2.5}{0.0025} = 1,000 \Omega = 1 \text{ k}\Omega$$

$$R_L = 1 \text{ k}\Omega$$

$$V_L = 2.5 \text{ V}$$

$$V_E \approx 1.1 \text{ V}$$

$$10-20\% \text{ of supply } V. \beta = \text{Gain} = \frac{I_C}{I_B}$$

$$V_{DC} = 5 \text{ V} \quad 10\% = 0.5 \text{ V}$$

$$20\% = 1.0 \text{ V, could be .9V, 1V, 1.1V}$$

$$V = IR, R = \frac{V}{I} = \frac{V_E}{I_E} = \frac{1.1 \text{ V}}{2.5 \text{ mA}} = \frac{1.1}{0.0025} = 440 \Omega$$


I only had a 470 Ω

$$V = IR, V_E = 2.5 \text{ mA} \cdot 470 \Omega = 1.175 \text{ V}$$

$$V_E = 1.1 \text{ V}$$



$$R_E = 470 \Omega$$
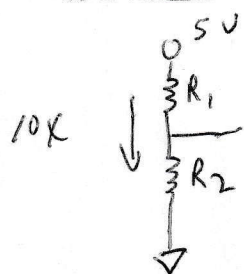
$$V_B = V_E + V_{EB} = 1.1 \text{ V} + 0.7 \text{ V} = 1.8 \text{ V}$$



$$\beta = \text{gain} \quad 100-300$$

$$\beta = 100$$

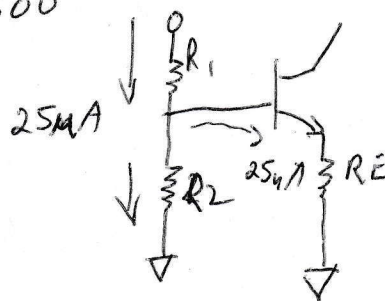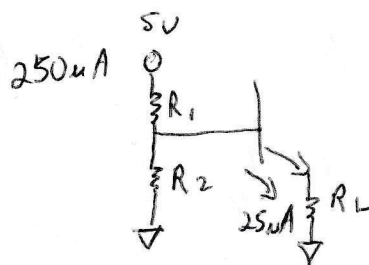

10%

The Amazing Semiconductor - Part 6 | Amplifier Design

3

$$I_C = 2.5 \text{ mA}$$

$$V_{DC} = 5 \text{ V}$$

$$V_B = 1.8 \text{ V}$$

$$\text{Assume } \beta = 100$$

$$I_B = \frac{I_C}{\beta}$$

$$\beta = \frac{I_C}{I_B}$$

$$I_B = \frac{2.5 \text{ mA}}{100}$$

$$I_B \beta = I_C$$

$$I_B = 25 \mu\text{A}$$

$$I_B = \frac{I_C}{\beta}$$

$$10 \times 25 \mu\text{A} = 250 \mu\text{A} = I_{\text{divider}}$$

$$I_{\text{divider}} = 250 \mu\text{A}$$

$$V = IR \quad R_2 = \frac{V_B}{I_{\text{divider}}} = \frac{1.8 \text{ V}}{250 \mu\text{A}} = 7.2 \text{ k}\Omega$$



$$R_1 = \frac{V_{DC} - V_B}{I_{\text{divider}}} = \frac{5 \text{ V} - 1.8 \text{ V}}{250 \mu\text{A}} = \frac{3.2 \text{ V}}{250 \mu\text{A}} = 12.8 \text{ k}\Omega$$

I chose:

$$R_1 = 10 \text{ k}\Omega$$

$$R_2 = 1 \text{ k}\Omega$$

$$R_3 = 10 \text{ k}\Omega$$

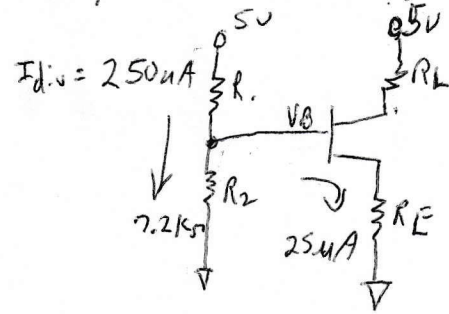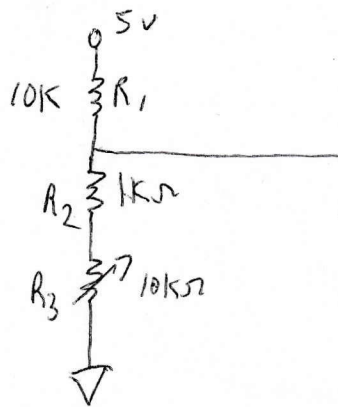

The Amazing Semiconductor - Part 6 | Amplifier Design (4)

LAB

Quick Recap:

- $V_{CC} = 5V$
- Q-Point = 2.5V
- $I_C = 2.5mA$ (we chose this value) $2.5mA = .0025A$
- $\beta = 100$ (we chose this value)
- $V_E = 1.1V \approx 10-20\%$ of V_{CC} , (went with $\approx 20\%$)
- $V_{BE} = 0.7V$ Ohm's LAW - $V = I \cdot R$, $R = \frac{V}{I}$

$$R_C = \frac{V_{CC} - V_C}{I_C} = \frac{5V - 2.5V}{0.0025A} = \frac{2.5V}{0.0025A} = 1000\Omega = \boxed{1K\Omega}$$

$$R_E = \frac{V_E}{I_E} = \frac{1.1V}{0.0025A} = \boxed{440\Omega} \text{ (Nearest Value } 470\Omega)$$

$$V_B = V_E + V_{BE} = 1.1V + 0.7V = \boxed{1.8V} \quad \beta = \frac{I_C}{I_B}, I_B = \frac{I_C}{\beta}$$

$$I_B = \frac{I_C}{\beta} = \frac{0.0025A}{100} = 0.000025A = \boxed{25\mu A}$$

$$I_{B,V} = 10 \times I_B = 10 \times 25\mu A = 10 \times 0.000025A = 0.000250A = \boxed{250\mu A}$$

$$R_2 = \frac{V_B}{I_{B,V}} = \frac{1.8}{0.00025A} = 7200\Omega = \boxed{7.2K\Omega}$$

$$R_1 = \frac{V_{CC} - V_B}{I_{B,V}} = \frac{5V - 1.8V}{0.000250A} = \frac{3.2V}{0.000250A} = 12800\Omega = \boxed{12.8K\Omega}$$

$$R_C = 1K\Omega$$

$$R_E = 440\Omega$$

$$R_1 = 12.8K\Omega$$

$$R_2 = 7.2K\Omega$$

calculated

LAB Values

$$R_C = 1K\Omega$$

$$R_E = 470\Omega$$

$$R_1 = 10K\Omega$$

$$R_2 = 1K\Omega + 10K\Omega \text{ variable resistor}$$

$$\beta = \frac{2V}{0.05V} = \boxed{40}$$

$$A_v = \frac{V_{out}}{V_{in}}$$

LAB Value

$$V_{CC} = 5.04V$$

$$Q = 2.5V$$

$$I_C = 2.54mA$$

$$V_E = 1.19V$$

$$V_{BE} = 0.67V$$

$$V_B = 1.88V$$

$$I_{B,V} = 300\mu A$$

$$I_B = 30\mu A$$

This is on BuildCircuitsWithRich.com
Whoo Buddy!!!