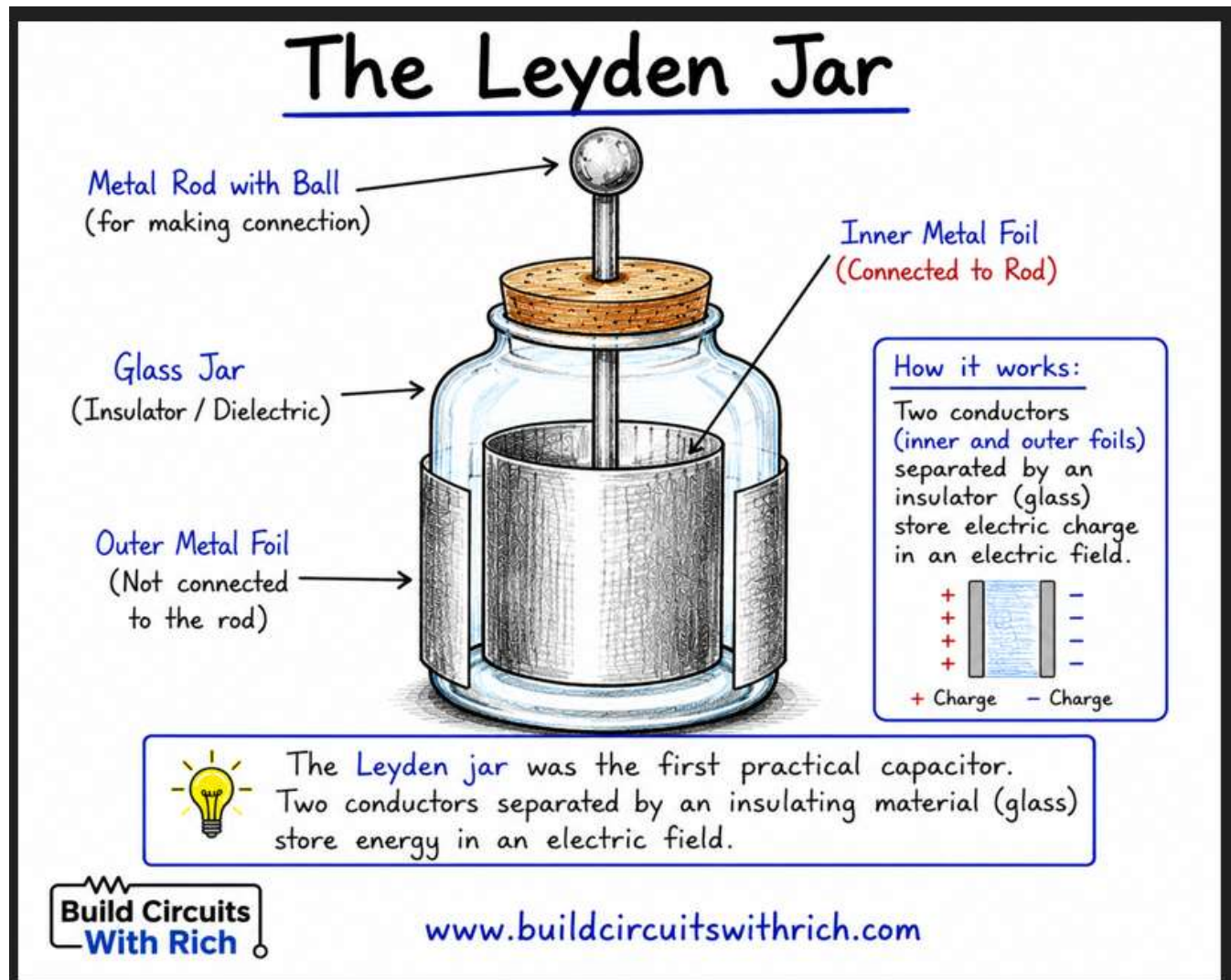


The Amazing Capacitor-Part 1 | What is a capacitor?

Friday, July 10, 2026 10:31 PM

The Amazing Capacitor - Part 1 [What is a capacitor?] BuildCircuitsWithRich.com



Michael Faraday

Born: September 22, 1791

Died: August 25, 1867 (age 75)

Nationality: English

Occupation: Physicist and chemist

Why is he important?

Michael Faraday made groundbreaking discoveries in electricity and magnetism. His work helped lay the foundation for electric motors, generators, transformers, and our understanding of electromagnetic fields.

Although he **did not invent the capacitor**, his research greatly advanced the understanding of capacitance and dielectrics.

The SI unit of capacitance—the farad (F)—is named in his honor.

Leyden Jar

Pieter van Musschenbroek

Born: March 14, 1692

Died: September 19, 1761 (age 69)

Nationality: Dutch

Occupation: Physicist, physician, mathematician, and professor

Why is he important?

Pieter van Musschenbroek is credited with developing one of the first practical capacitors—the **Leyden jar**—in 1746 while working at Leiden University in the Netherlands. His experiments showed that electrical charge could be stored and later released, laying the foundation for the modern capacitor. Around the same time, Ewald Georg von Kleist independently built a similar device.


1 micro farad = $1/1,000,000$ F

1 nano farad = $1/1,000,000,000$ F

1 pico farad = $1/1,000,000,000,000$ F

The Capacitor

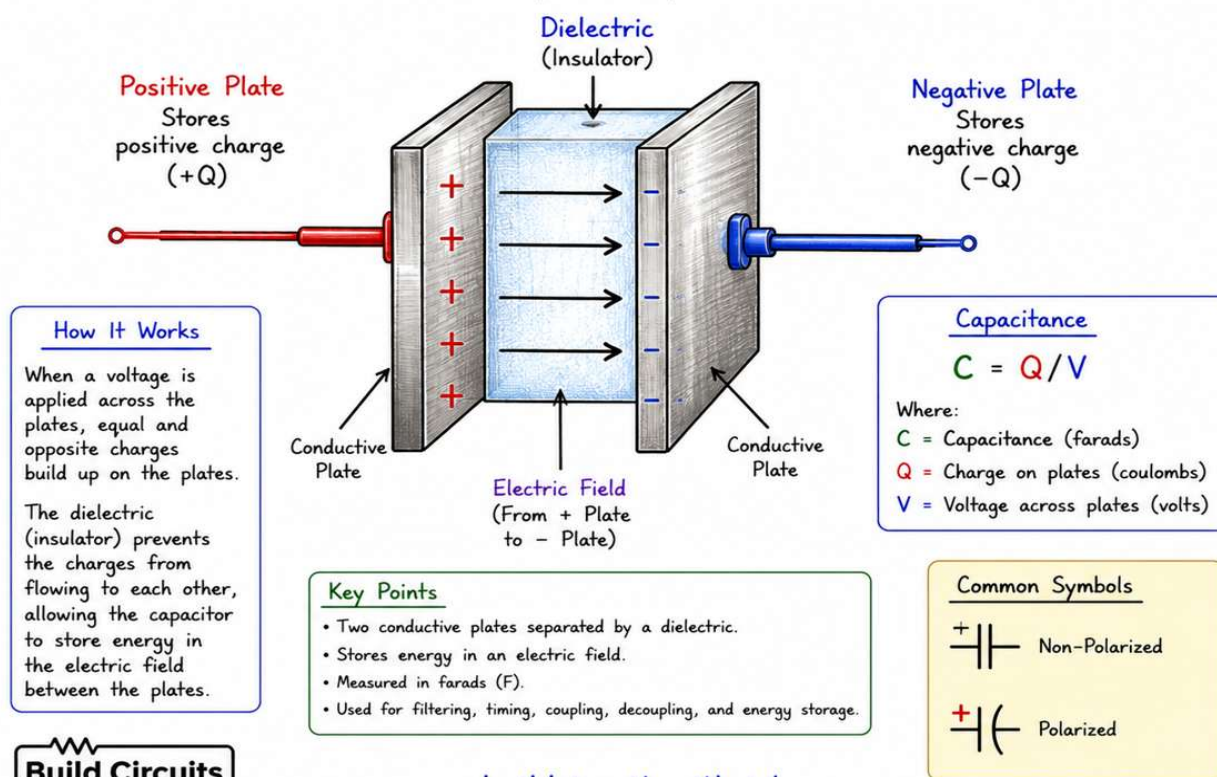Two Conductive Plates Separated by an Insulator (Dielectric)



**Build Circuits
With Rich**

www.buildcircuitwithrich.com

What Affects Capacitance?

Capacitance (C) depends on three things:
Plate Area (A), Distance Between Plates (d), and Dielectric (ϵ_r)


Formula:

$$C = \epsilon_r \epsilon_0 \frac{A}{d}$$

(ϵ_0 = constant)

1 Plate Area (A)


Bigger area = More capacitance

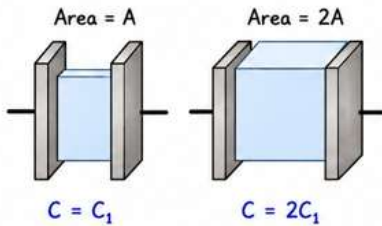

Double the area,
double the capacitance.

2 Distance Between Plates (d)


Smaller distance = More capacitance

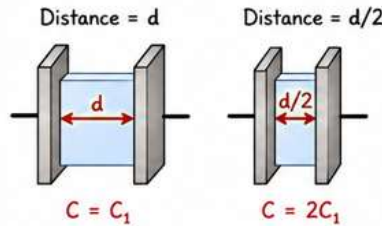

Cut the distance in half,
double the capacitance.

3 Dielectric (ϵ_r)

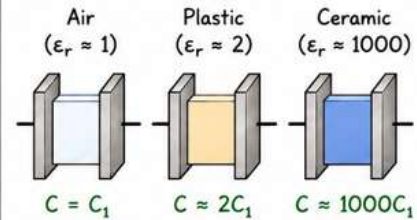
Better dielectric (higher ϵ_r) =
More capacitance



Higher ϵ_r ,
more capacitance.

In Short:

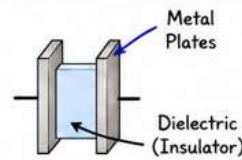- Bigger plate area (A) → More capacitance
- Smaller distance (d) → More capacitance
- Higher dielectric (ϵ_r) → More capacitance




Build Circuits
With Rich

Lab

RC CIRCUIT: CAPACITOR CHARGING

THE CIRCUIT

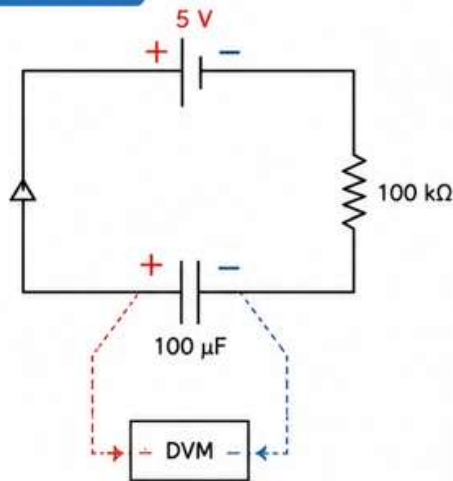


COMPONENTS

- 5 V DC Power Supply
- 100 kΩ Resistor
- 100 μF Capacitor
- Digital Voltmeter (DVM)

HOW IT WORKS

- 1 When power is applied, the capacitor charges through the 100 kΩ resistor.
- 2 The voltage across the capacitor (V_C) rises over time.
- 3 The DVM measures the voltage across the capacitor.
- 4 When power is removed, the capacitor can discharge through a resistor.

CAPACITOR VOLTAGE vs. TIME

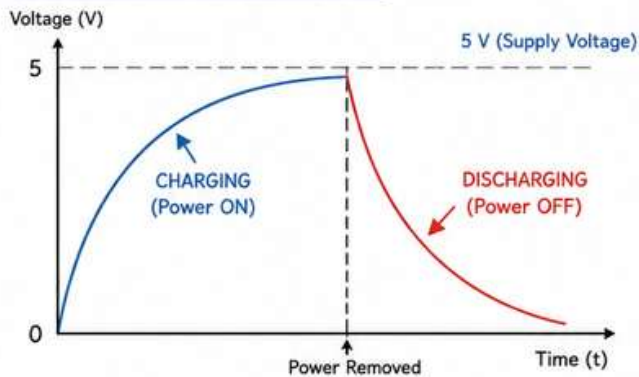

KEY EQUATIONS

Time Constant (τ)

$$\tau = R \times C$$

Charging Equation

$$V_C(t) = V_S \left(1 - e^{-t/\tau} \right)$$

Discharging Equation

$$V_C(t) = V_0 - e^{-t/\tau}$$

R = Resistance (ohms)

C = Capacitance (farads)

V_S = Supply Voltage (volts)

V_0 = Initial Voltage on Capacitor

KEY TAKEAWAYS



A capacitor stores energy in an electric field between its plates.



The resistor limits current and controls how fast the capacitor charges or discharges.



The time constant ($\tau = RC$) determines how quickly the voltage changes.



The capacitor does not charge instantly. It charges quickly at first, then slows down.



Capacitors can remain charged after power is removed.



Practical Tip: Always discharge capacitors safely through a resistor before handling them. Never short a capacitor directly with a wire or screwdriver.