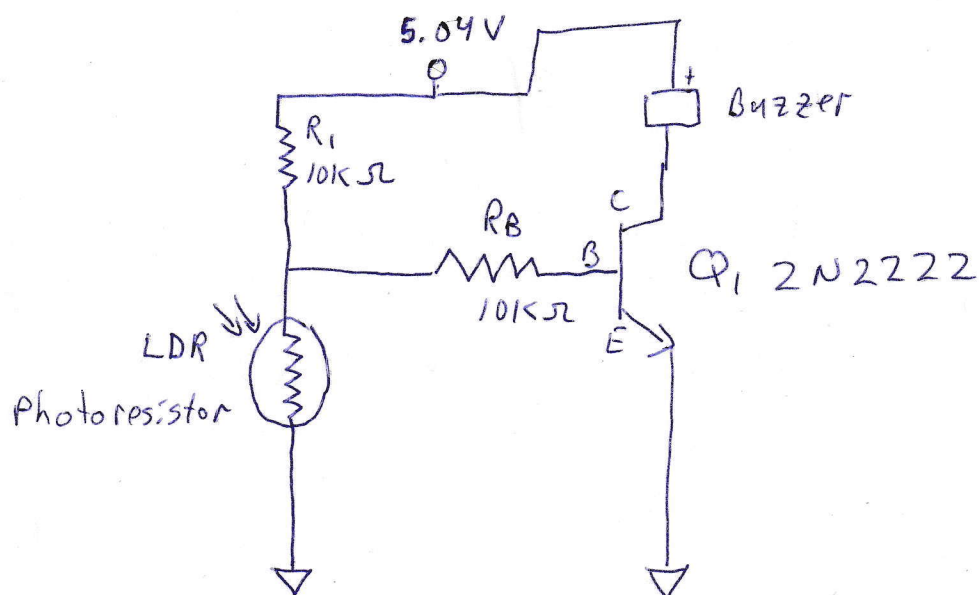


Build a Simple Shadow Alarm

John 8:12

	Calculated	Measured
V _{NODE} (Light)	0.46 V	0.47 V
V _{NODE} (Shadow)	2.52 V	1.42 V
V _{Base} (shadow)		0.65 V

Build Circuits With Rich LAB NOTES



LDR = Light-Dependent Resistor

buildcircuitswithrich.com